

Lecture 4

Sequential units. Registers

Computing platforms, semester 2

Novosibirsk State University
University of Hertfordshire

D. Irtegov, A.Shafarenko


2019

Some terminology

- Combinational units: pure logical functions.
 - Output depends only on input
 - No side effect (except delay)
 - Can be described by single logical expression
- Sequential units: have internal state
 - Output depends not only on the inputs
 - Input can have side-effect (changing internal state)
 - Depend on timing
 - Require triggers, latches and memory


Some final words on combinatory circuits

x	y	z	out
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	0

 

Implementing arbitrary truth table

- Draw input lines. Also add inverted lines
- For every row yielding 1, add AND gate and connect it to corresponding input lines (may be to inverted one)
- Connect outputs of AND gates to OR gate
- This is called minterm approach (normal disjunctive form)
- FPGA design tools do this automatically
- Optimization steps (optional)
 - If table has more rows yielding 1 than 0, build device for inverted table and invert the output
 - Delete unused direct or inverted input lines

 

$$Q = AB + (B+C) * BC$$

By distributing the BC into (B+C) we get:

$$Q = AB + (BBC + CBC)$$

Using the multiplicative idempotent law again we know that $B*B = B$ and that $C*C=C$ so we get:


$$Q = AB + (BC + BC)$$

Using the additive idempotent law ($B + B = B$) we get:


$$Q = AB + BC$$

By factoring out the B, we get the final answer of


$$Q = B(A+C)$$

 


Edge detector

 

 
- One of the simplest sequential devices
- Detects input transition from low to high
- Generates pulse when transition occurs




Edge detector

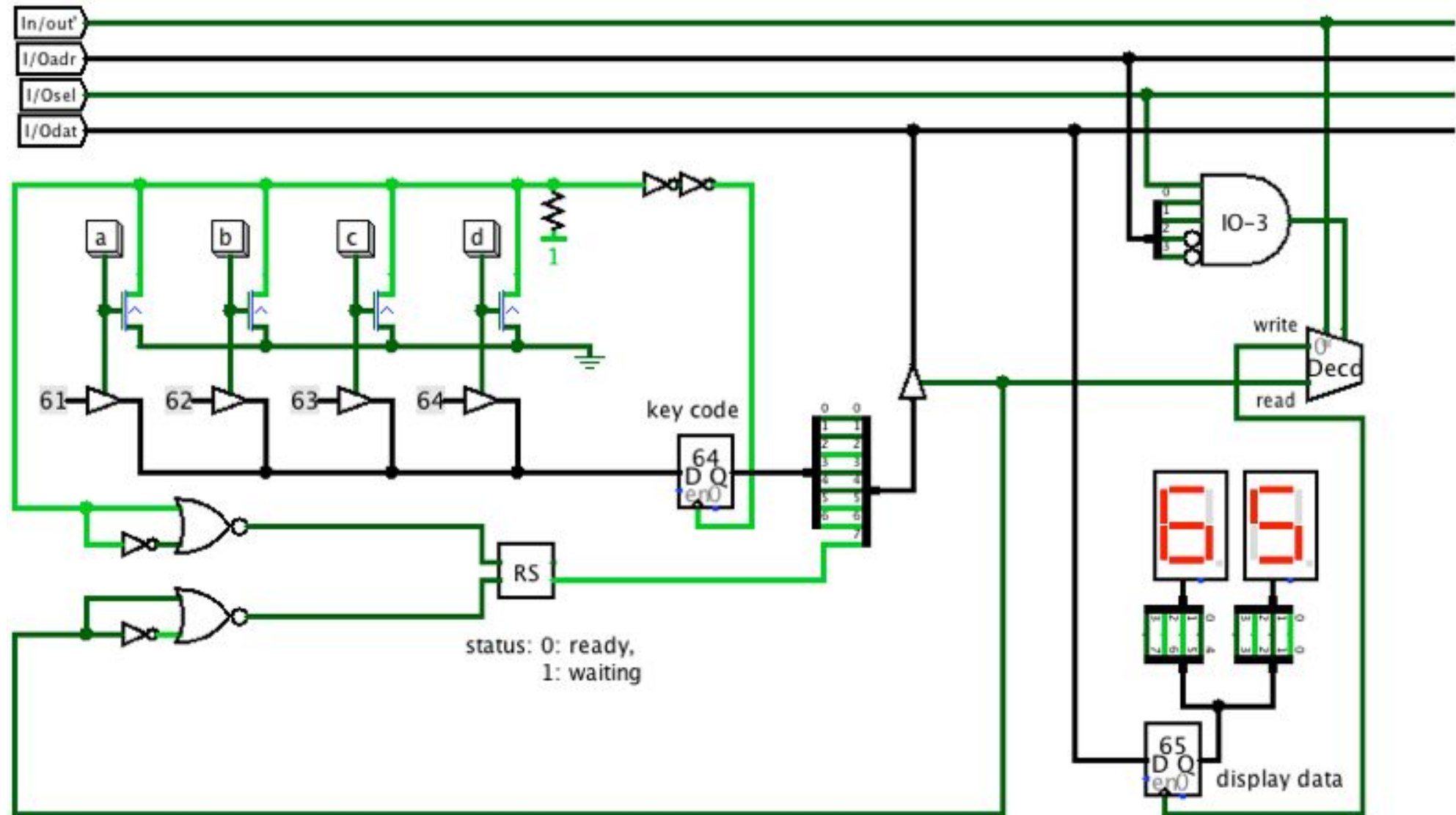

Flip-flop


 


S	R	Q	\bar{Q}
0	0	Режим хранения информации	
0	1	0	1
1	0	1	0
1	1	Запрещенное состояние	

 

- Also known as Set-Reset trigger, RS-trigger, RS-latch, etc
- Detects and remembers change in R and S signals
- Edge-triggered (like edge detector)

D-trigger

  

- Remembers value of D when clock is high
- When D changes on high clock, we have problem


D-trigger in Logisim

Передний фронт;


Задний фронт;

Высокий уровень;

Низкий уровень.

 


Master-slave latch

 


- Two D-triggers connected sequentially, with inverted clock
- First trigger latches D on high clock
- Second trigger latches stable value of (Q) on low clock


MSL timing diagram

 

T-trigger

 

JK-trigger

 


ВХОДЫ			ВЫХОДЫ		Режим работы
C	J	K	Q	\overline{Q}	
0	x	x	Q	\overline{Q}	Хранение
	0	0	Q	\overline{Q}	
↓	0	1	0	1	Запись 0
	1	0	1	0	Запись 1
	1	1	\overline{Q}	Q	Иверсия

Other interesting devices


- Edge-triggered D-latch
<http://www.falstad.com/circuit/e-edgedff.html>
- JK-trigger <http://www.falstad.com/circuit/e-jkff.html>
- 4-bit ripple counter built on JK-triggers
<http://www.falstad.com/circuit/e-counter.html>
- 4-bit synchronous counter (simplified carry lookahead)
<http://www.falstad.com/circuit/e-synccounter.html>
- Decimal (BCD) counter
<http://www.falstad.com/circuit/e-deccounter.html>

D-latch using CMOS PTL

 


- Six transistors
- The D-latch on logic gates used 22 transistors!

Master-slave latch on PTL

 

Multiported register

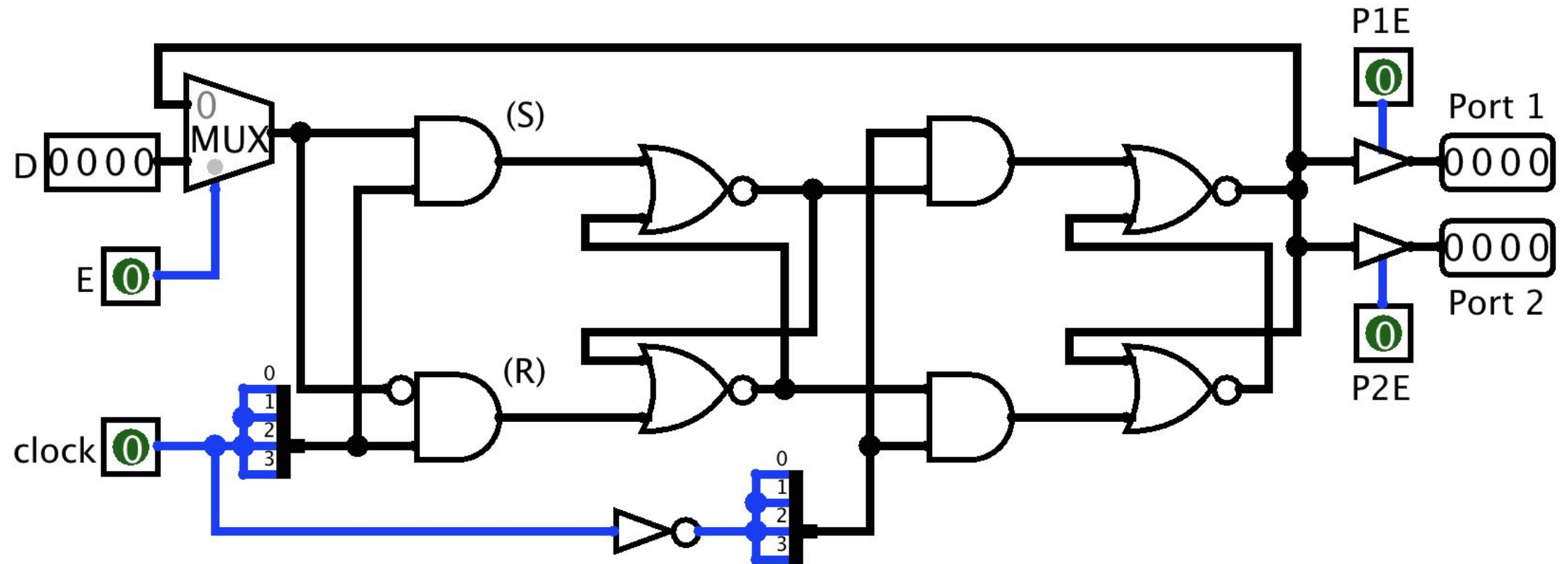


Multiport register features


- Multibit storage (4 bit on previous slide)
- Controlled latching. Has clock and Enable signals.
 - In CdM-8, most instructions operate on a single register.
 - Other registers must remain unchanged.
- Multiple three-state outputs
 - In CdM-8, only selected register values are needed on each clock
 - Using three-state outputs, we can attach all registers to a single bus or to several buses

Finite state machine

 
- A formal computation model
- Used in many branches of computing
 - Network protocols
 - Parsers and lexers
 - Event-driven programming
 - Hardware design
 - etc
- Formally, any digital device (including von Neumann computer) is a Finite State Machine
- Can be represented as graph of states and transitions
- Can be directly implemented in hardware




Hardware FSM

 

One possible next step: microprogramming

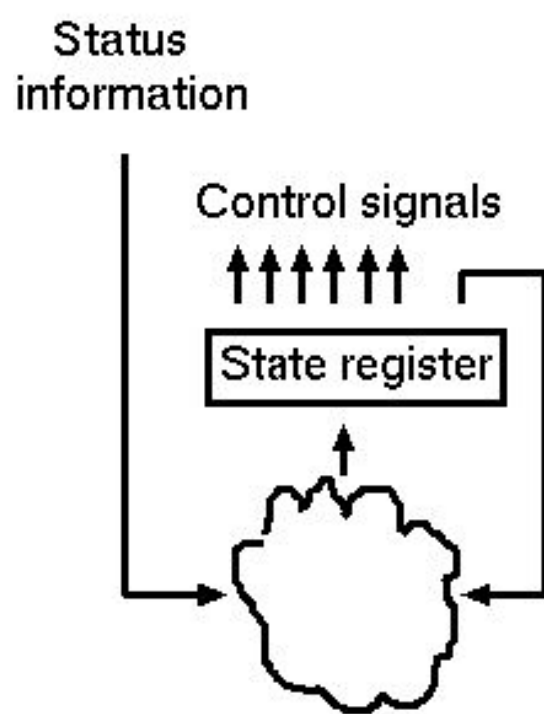

(a) Hardwired control

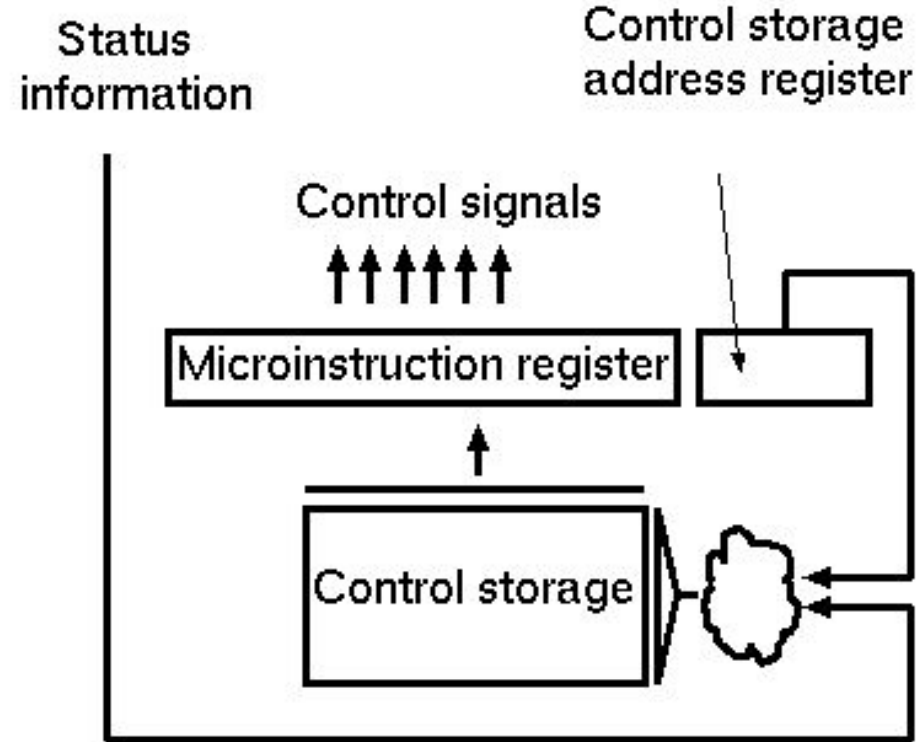

(b) Microprogrammed control

Microprogramming

- Most modern CPU are actually microprogrammed machines
- Many peripheral computer devices (those which do not have it's own CPU inside) also are implemented as microprogrammed machines or FSM
- But we won't go into this now